
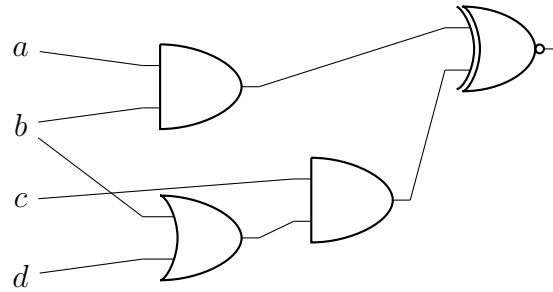


Name:

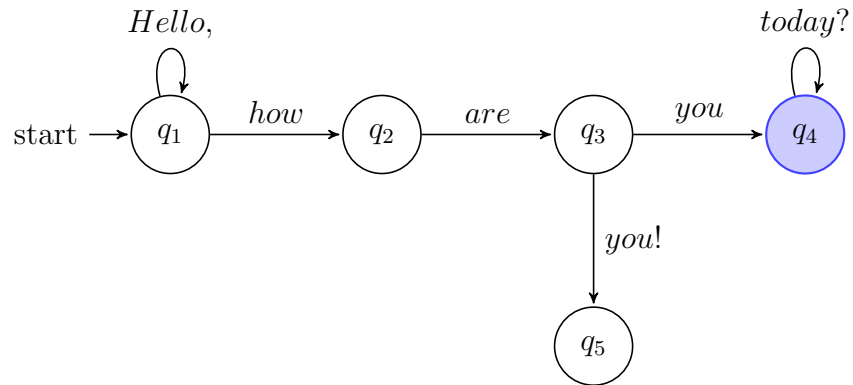1. RECAP: What values of (a,b,c,d) make this logic circuit output a false value?



2. Describe in words or in a regular expression what strings this automata will accept. You can write each word in parentheses like *(Hello)* so you can treat it like a single character.



3. Write an automata that will accept strings starting with an R and then followed by zero or more h 's. Such as R , Rh , Rhh ,...

4. Describe what the $HALT(\#_p, x)$ program could do if anyone could ever write it.